



جامعة برج العرب التكنولوجية
BORG AL ARAB TECHNOLOGICAL UNIVERSITY




Digital Engineering

Assoc. Prof. Osama Elnahas, Dr. Dina Abdelhafiz
Dr. Bassant Tolba, Dr. Radwa Rady

Second Year –Information Technology Program
Fall 2025

Lecture (2)

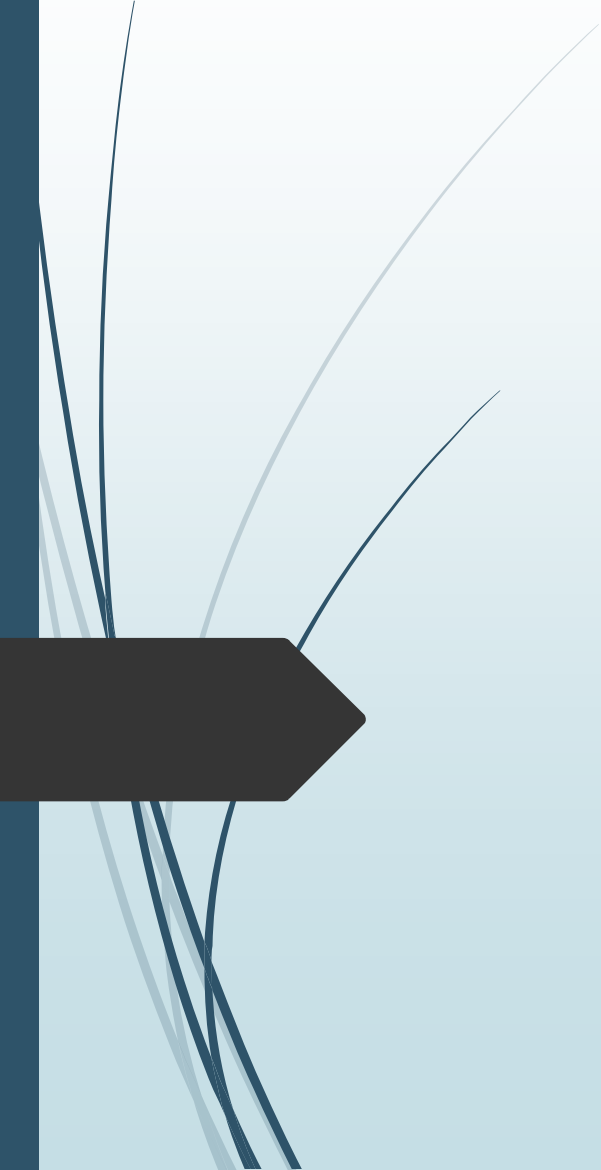



3


Part A

Basic Gates

Basic Gates

► **Unary gate:** A **NOT** gate is sometimes referred to as an *inverter* because it inverts the input value

NOT (Inverter)

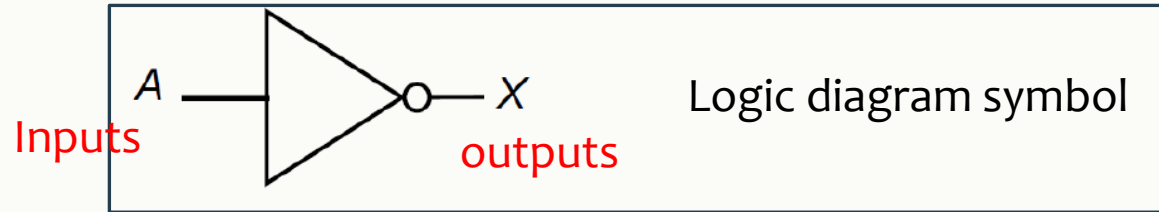

$$X = \bar{A}$$

Boolean expression

$$X = A'$$

A NOT gate is sometimes referred to as an inverter because it inverts the input value

A	X
0	1
1	0


Truth table

Basic Gates

The *Output* signal from an **AND** gate is 1 (ON) if and only if **both** *Input* signals are 1.

► Unary and binary gates:

NOT (Inverter)

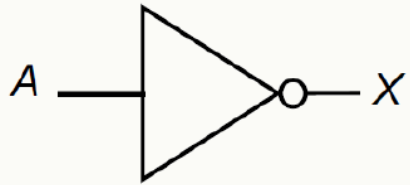


$$X = \bar{A}$$

$$X = A'$$

A	X
0	1
1	0

AND

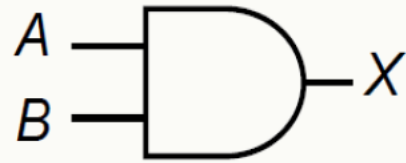

Logic diagram symbol

$$X = A \cdot B$$

Boolean expression


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

Truth table

Basic Gates

► Unary and binary gates:

NOT (Inverter)

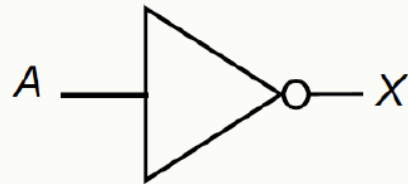


$$X = \bar{A}$$

$$X = A'$$

A	X
0	1
1	0

AND

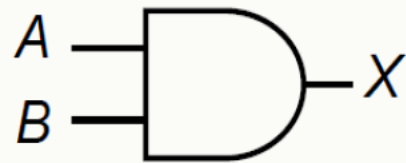


$$X = A \cdot B$$

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

The Output signal from an **OR** gate is on, 1 if either, or both, Input signals are on, 1.

OR

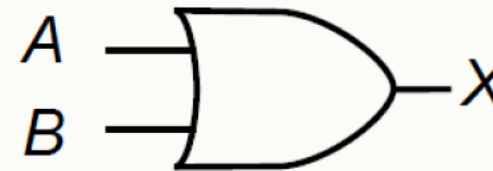

Logic diagram symbol

$$X = A + B$$

Boolean expression

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1


Truth table

Basic Gates

■ The Output from an **XOR** (exclusive or) is *True* (on, 1) if and only if the *Input* signals are different..

■ Unary and binary gates:

NOT (Inverter)

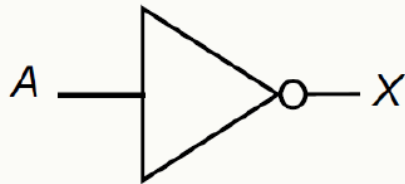


$$X = \bar{A}$$

$$X = A'$$

A	X
0	1
1	0


AND

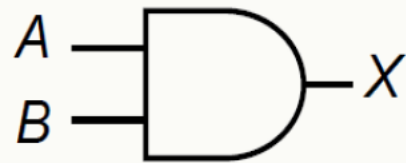

$$X = A \cdot B$$

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

OR

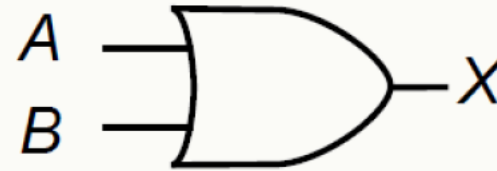


$$X = A + B$$

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

Logic diagram symbol

XOR

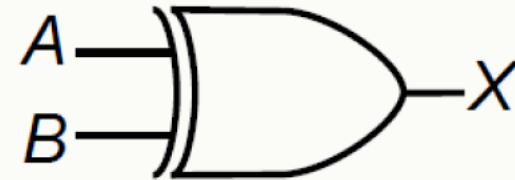

Exclusive OR

$$X = A \oplus B$$


Boolean expression

Truth table


A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Basic Gates

► With 3 inputs: Guess the outputs ??

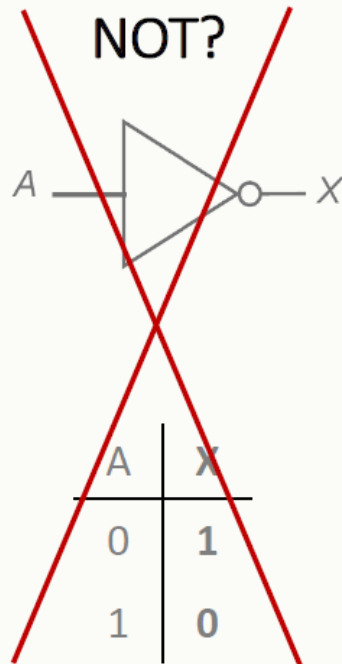


AND

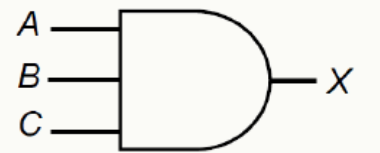

A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$$X = A \cdot B \cdot C$$


OR

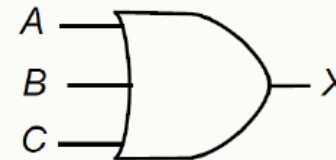

A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$$X = A + B + C$$

XOR

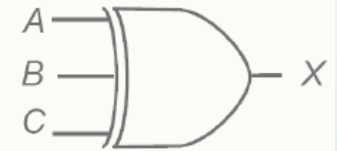


A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


$$X = A \oplus B \oplus C$$

Basic Gates

► With 3 inputs: Guess the outputs ??

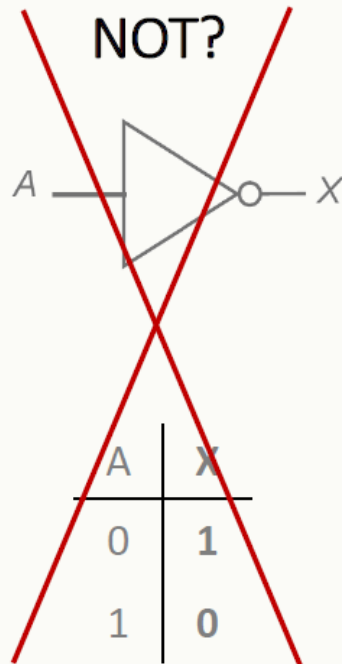


AND

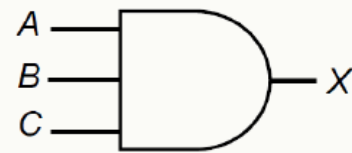

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$X = A \cdot B \cdot C$$


OR

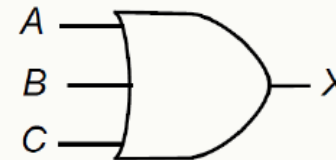

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$X = A + B + C$$

XOR

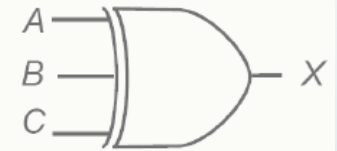


A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


$$X = A \oplus B \oplus C$$

Basic Gates

► With 3 inputs: Guess the outputs ??

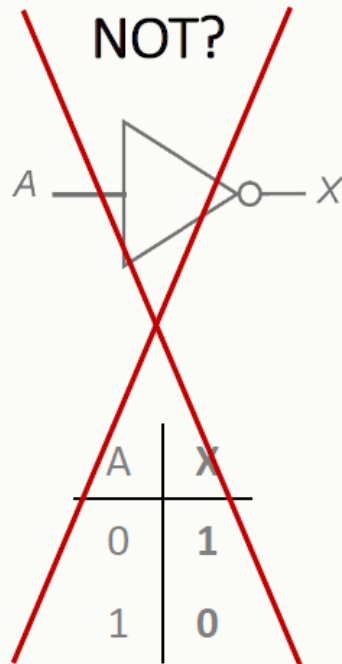


AND

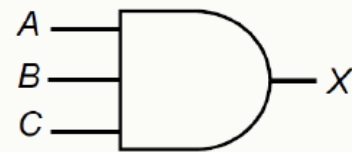

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$X = A \cdot B \cdot C$$

OR

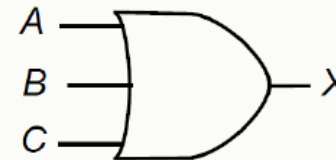

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$X = A + B + C$$

XOR




A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


$$X = A \oplus B \oplus C$$

Basic Gates

► With 3 inputs:

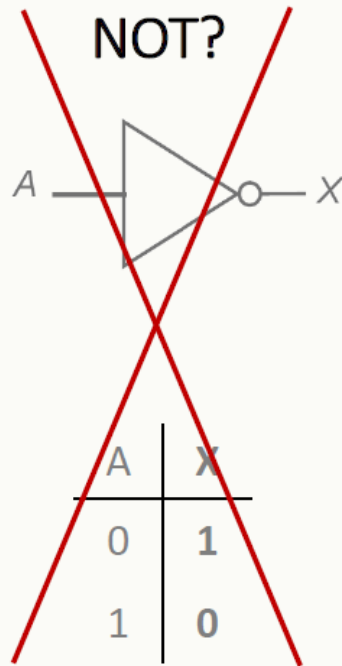


AND

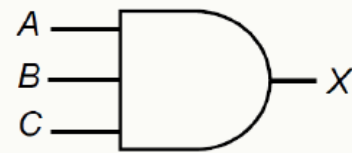

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$X = A \cdot B \cdot C$$


OR

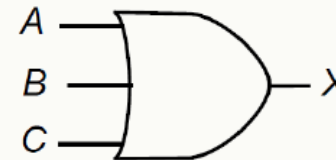

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$X = A + B + C$$

XOR

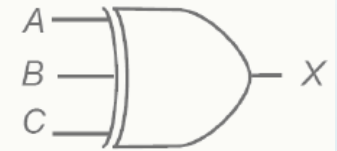


A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$X = A \oplus B \oplus C$$

Inverted Basic Gates

► Buffer: Inverted NOT:

NOT


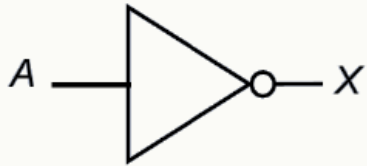


A	X
0	1
1	0

Digital Engineering Fall 2025

$$X = \bar{A}$$

“Buffer”

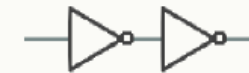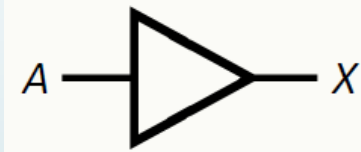


A	X
0	0
1	1

$$X = A$$

Inverted Basic Gates

► NAND: Inverted AND:

AND

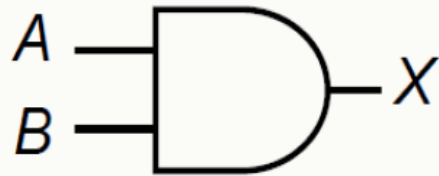


<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1

Digital Engineering Fall 2025

$$X = A \cdot B$$

NAND

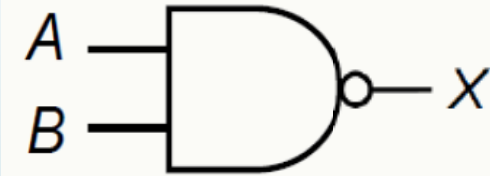


<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	1
1	0	1
1	1	0

$$X = \overline{A \cdot B}$$

10/3/2025


Inverted Basic Gates

► NOR: Inverted OR:

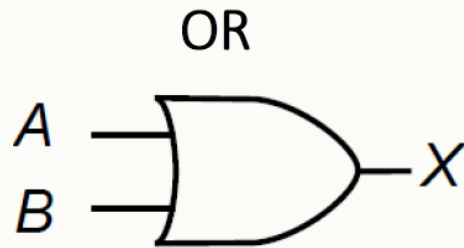

<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	1

$$X = A + B$$

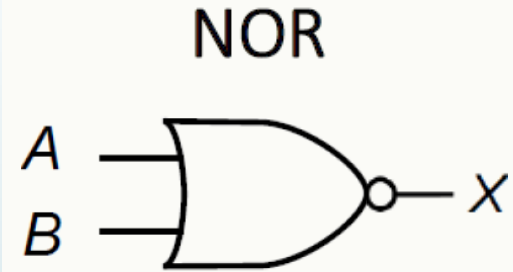


<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	0

$$X = \overline{A + B}$$

Inverted Basic Gates

Exclusive NOR: Inverted XOR


Are they different?

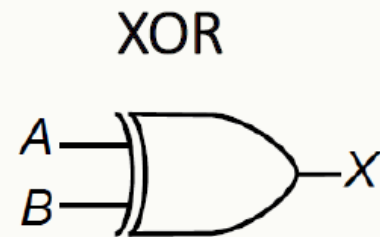

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

$$X = A \oplus B$$

Are they similar?

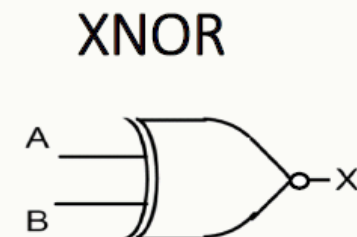


A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

$$X = \overline{A \oplus B}$$


Inverted Basic Gates

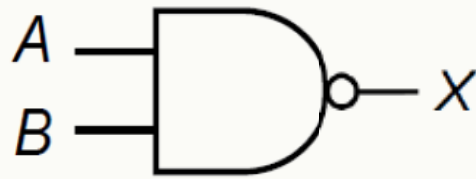- NAND: What if we connected the same input?
- Truth table?



<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	1
1	0	1
1	1	0


Digital Engineering Fall 2025

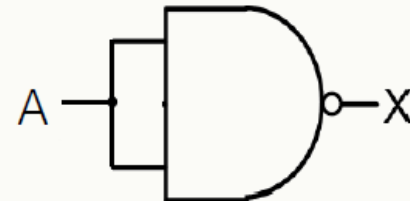

<i>A</i>	<i>A</i>	<i>X</i>
0	0	1
0	1	1
1	0	1
1	1	0


Inverted basic gates

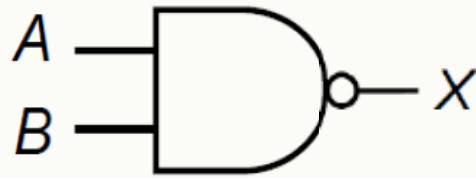- NAND: What if we connected the same input?
- Truth table?



<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	1
1	0	1
1	1	0


Digital Engineering Fall 2025

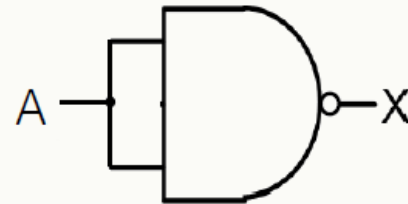

<i>A</i>	<i>A</i>	<i>X</i>
0	0	1


Inverted Basic Gates

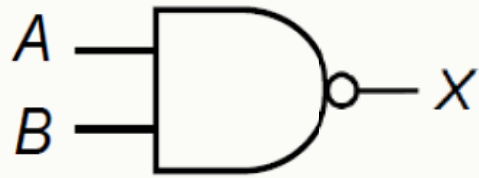- NAND: What if we connected the same input?
- Truth table?
- It will act as NOT gate (NAND and NOR gates are cheaper).




A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Digital Engineering Fall 2025

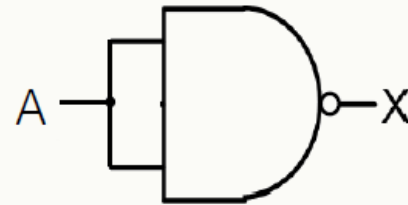

A	A	X
0	0	1
1	1	0

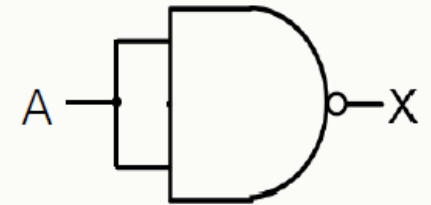

A	X
0	1
1	0

10/3/2025

Summary

1. AND Gate

Expression: $Y = A \cdot B \cdot C$

(Outputs true only when all inputs are true.)

2. OR Gate

Expression: $Y = A + B + C$

(Outputs true if at least one input is true.)

3. NOT Gate

Expression: $Y = \overline{A}$

(Outputs the inverse of the single input.)

4. NAND Gate

Expression: $Y = \overline{A \cdot B \cdot C}$

(Outputs false only when all inputs are true.)

Digital Engineering Fall 2025

5. NOR Gate

Expression: $Y = \overline{A + B + C}$

(Outputs true only when all inputs are false.)

6. XOR Gate

Expression: $Y = A \oplus B \oplus C$

(Outputs true if an odd number of inputs are true.)

7. XNOR Gate

Expression: $Y = \overline{A \oplus B \oplus C}$

(Outputs true if an even number of inputs are true.)


Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (1): Convert into notation: Give the output a symbol X

$$X = (\overline{A \cdot B}) \cdot (A + B)$$

- Step (2): Draw circuit diagram:

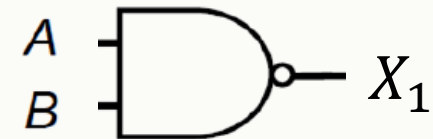- Start with each ().
- Draw the NAND gate.
- $X_1 = \overline{A \cdot B}$



Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (1): Convert into notation: Give the output a symbol X


$$X = (\overline{A \cdot B}) \cdot (A + B)$$

- Step (2): Draw circuit diagram:

- Start with each ().

- Draw the OR gate.

- $X_2 = (A + B)$

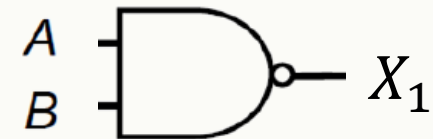

Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (1): Convert into notation: Give the output a symbol X


$$X = (\overline{A \cdot B}) \cdot (A + B)$$

- Step (2): Draw circuit diagram:

- AND between X_1, X_2

- $X = X_1 \cdot X_2$

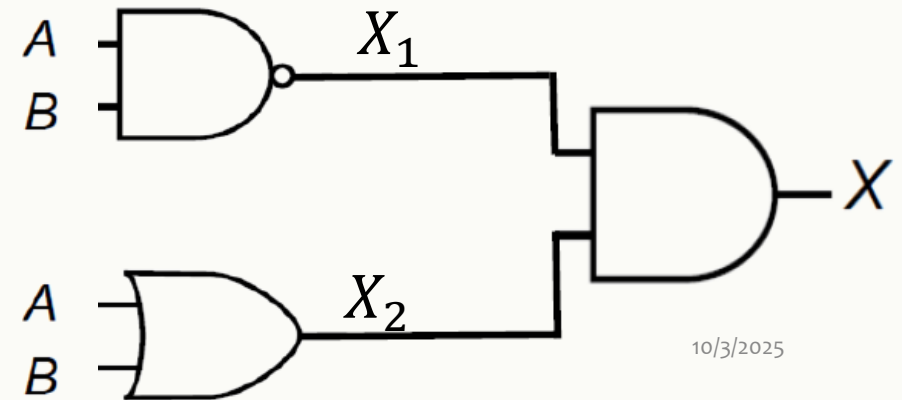- $X = (\overline{A \cdot B}) \cdot (A + B)$




Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (1): Convert into notation: Give the output a symbol X


$$X = (\overline{A \cdot B}) \cdot (A + B)$$

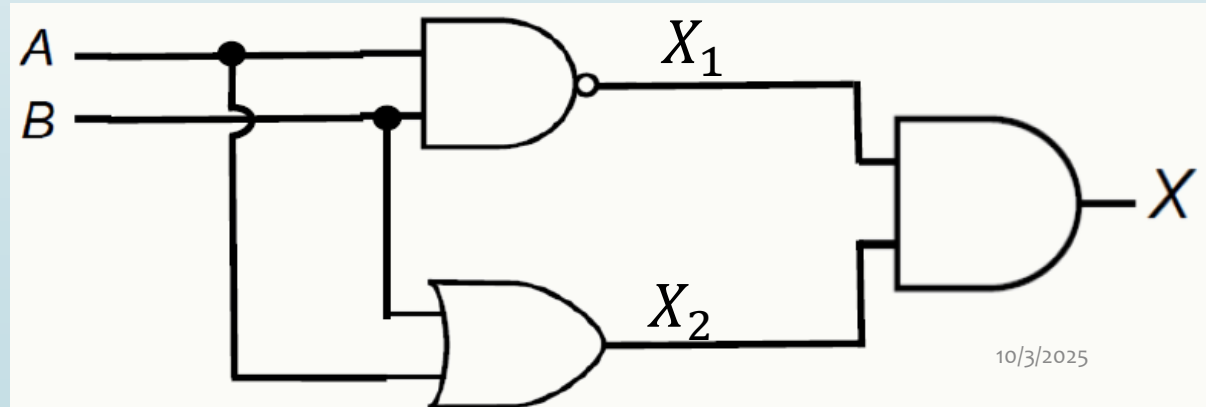- Step (2): Draw circuit diagram:
 - Optimize figure.



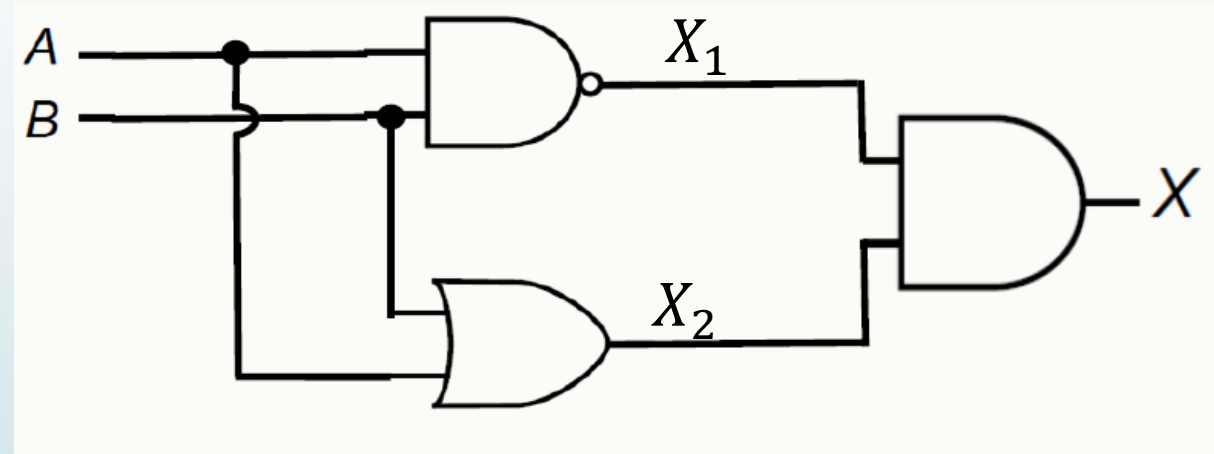Question ??


- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (3): Truth table of X:
 - Truth table of X_1 = ??
 - $X_1 = (\overline{A \cdot B})$



$A \text{ NAND } B$		
A	B	X_1
0	0	
0	1	
1	0	
1	1	

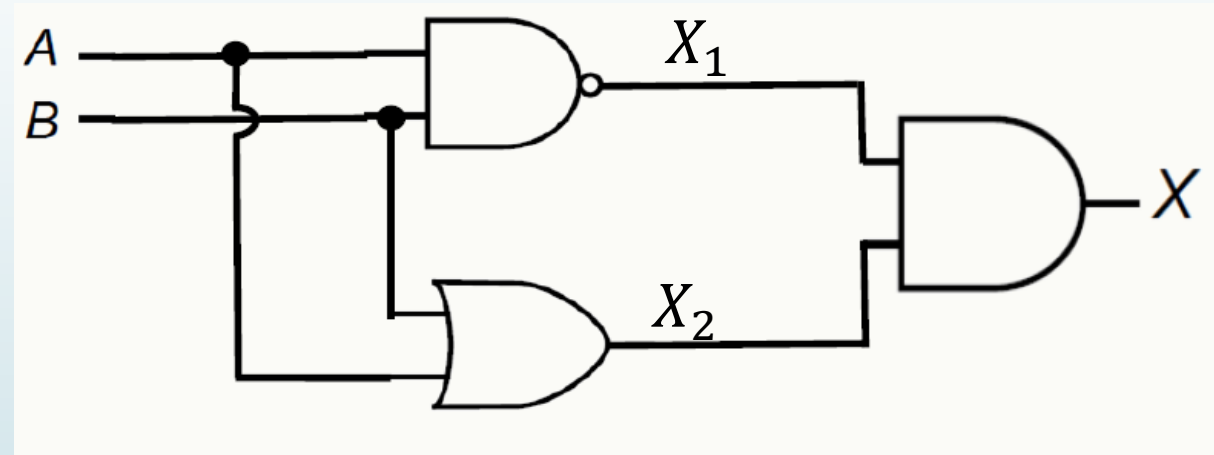Question ??


- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (3): Truth table of X:
 - Truth table of X_1 = ??
 - $X_1 = (\overline{A \cdot B})$



$A \text{ NAND } B$		
A	B	X_1
0	0	1
0	1	1
1	0	1
1	1	0

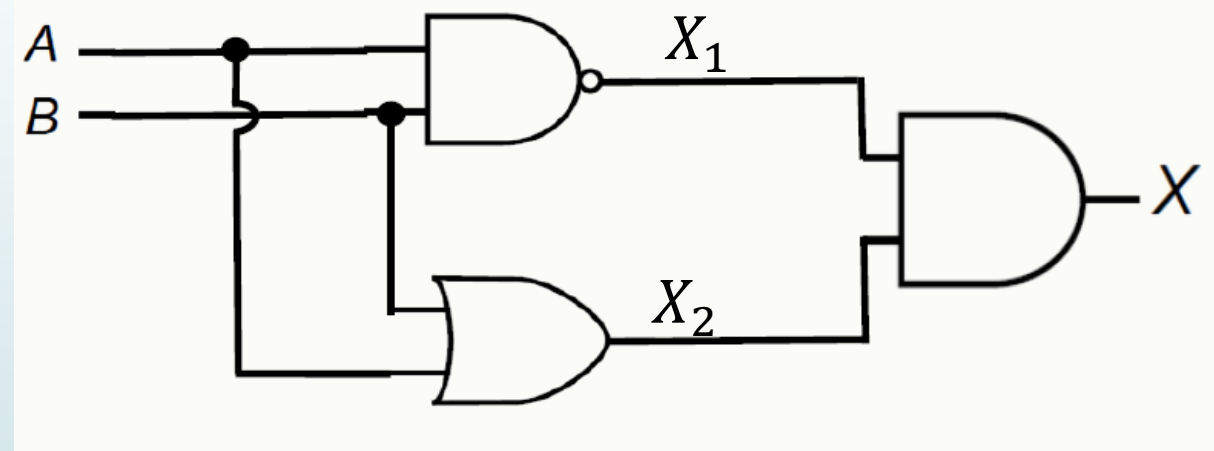Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (3): Truth table of X:
 - Truth table of X_2 = ??
 - $X_2 = A + B$




$A \text{ NAND } B$		
A	B	X_1
0	0	1
0	1	1
1	0	1
1	1	0

Digital Engineering Fall 2025

$A \text{ OR } B$		
A	B	X_2
0	0	
0	1	
1	0	
1	1	

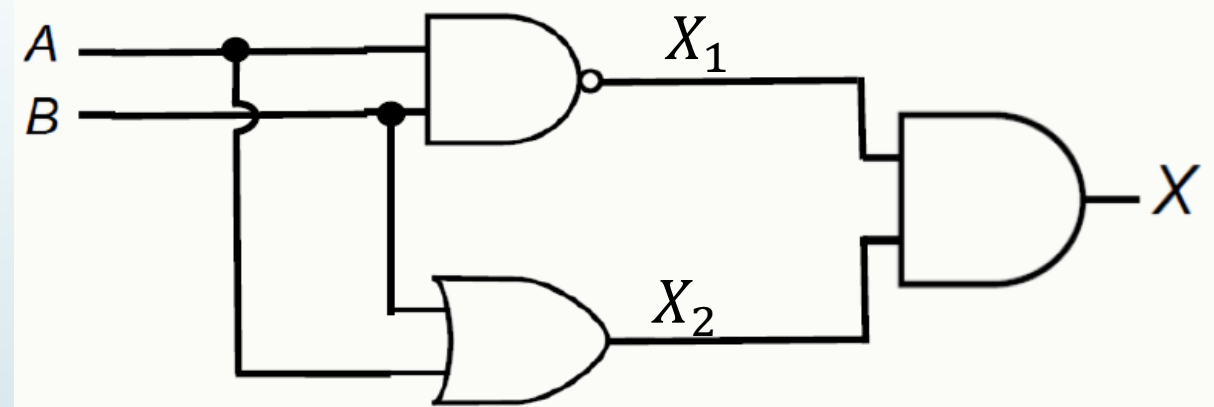Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (3): Truth table of X:
 - Truth table of X_2 = ??
 - $X_2 = A + B$




$A \text{ NAND } B$		
A	B	X_1
0	0	1
0	1	1
1	0	1
1	1	0

Digital Engineering Fall 2025

$A \text{ OR } B$		
A	B	X_2
0	0	0
0	1	1
1	0	1
1	1	1

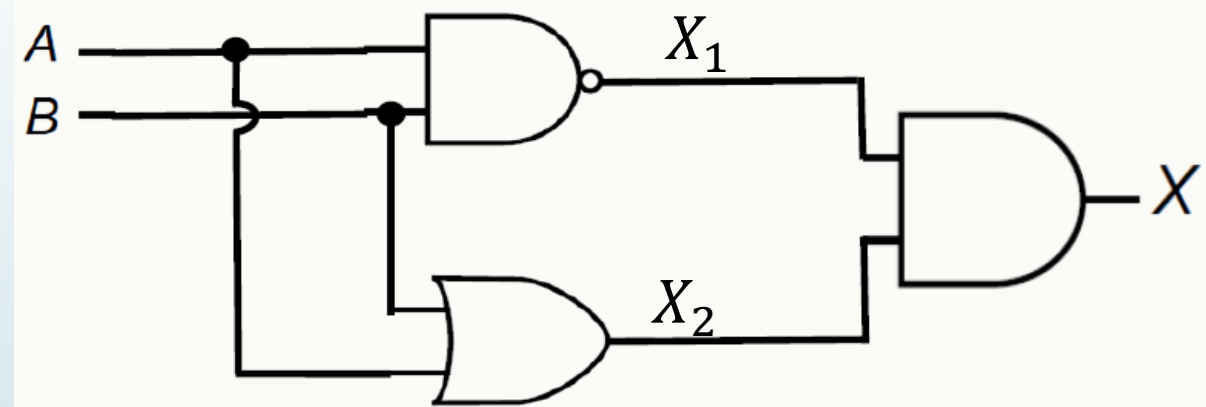Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (3): Truth table of X:
 - Truth table of $X = ??$
 - $X = X_1 \cdot X_2$



$A \text{ NAND } B$		
A	B	X_1
0	0	1
0	1	1
1	0	1
1	1	0


Digital Engineering Fall 2025

$A \text{ OR } B$		
A	B	X_2
0	0	0
0	1	1
1	0	1
1	1	1

A	B	X_1	X_2	X
0	0	1	0	
0	1	1	1	
1	0	1	1	
1	1	0	1	

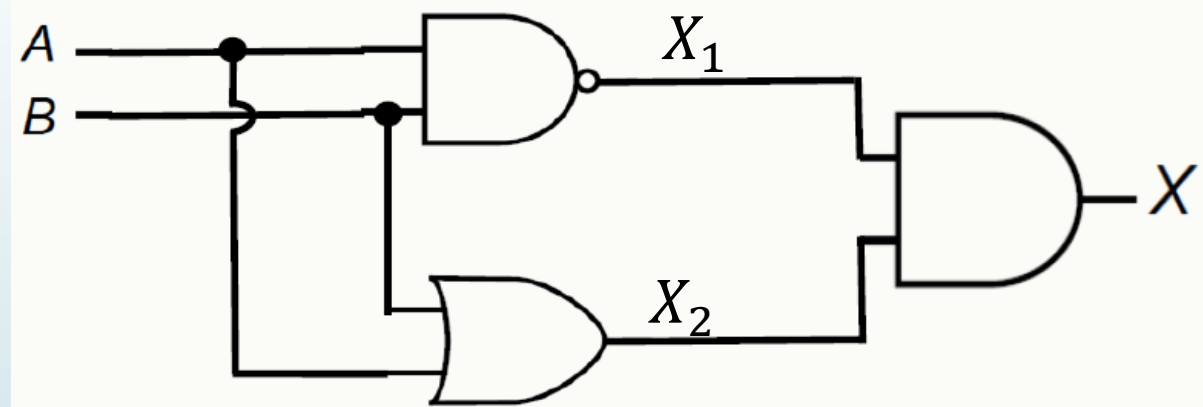Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (3): Truth table of X:
 - Truth table of $X = ??$
 - $X = X_1 \cdot X_2$



$A \text{ NAND } B$		
A	B	X_1
0	0	1
0	1	1
1	0	1
1	1	0


Digital Engineering Fall 2025

$A \text{ OR } B$		
A	B	X_2
0	0	0
0	1	1
1	0	1
1	1	1

A	B	X_1	X_2	X
0	0	1	0	0
0	1	1	1	1
1	0	1	1	1
1	1	0	1	0

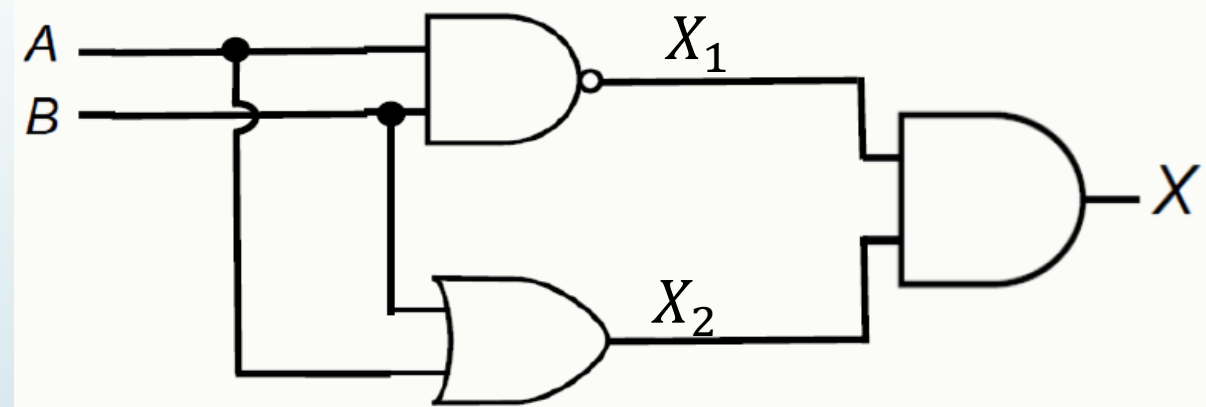Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (3): Truth table of X:
 - Summary:



<i>A NAND B</i>		
<i>A</i>	<i>B</i>	<i>X₁</i>
0	0	1
0	1	1
1	0	1
1	1	0

Digital Engineering Fall 2025

<i>A OR B</i>		
<i>A</i>	<i>B</i>	<i>X₂</i>
0	0	0
0	1	1
1	0	1
1	1	1

<i>A</i>	<i>B</i>	<i>X₁</i>	<i>X₂</i>	<i>X</i>
0	0	1	0	0
0	1	1	1	1
1	0	1	1	1
1	1	0	1	0

<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

19/3/2025

Question ??

- Which logic gate is “(A NAND B) AND (A OR B)” equivalent to?
- Step (4): Compare the known truth tables of AND, OR, NOR, NAND.
 - It is the truth table of XOR.

$$X = A \oplus B \text{ (XOR)}$$

<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

Part B

Boolean Algebra (Switching Algebra)

Operations with 0

■ From the AND truth table:

■ Any AND with zero is zero.

■ $0 \cdot X = X \cdot 0 = 0$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

■ From the OR truth table:

■ The OR of any value with zero is the same value.

■ $0 + X = X + 0 = X$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Operations with 1

► From the AND truth table:

► The AND of any value with 1 is the same value

► $1 \cdot X = X \cdot 1 = X$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

► From the OR truth table:

► Any OR with 1 is 1

► $1 + X = X + 1 = 1$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Idempotent

■ The operation of a variable with itself:

■ From the AND truth table:

■ $X \cdot X = X$

■ From the OR truth table:

■ $X + X = X$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Complementarity

- The operation of a variable with its complement:
- From the AND truth table:

$$\Rightarrow X \cdot \bar{X} = 0$$

- From the OR truth table:

$$\Rightarrow X + \bar{X} = 1$$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Simple Laws

■ Involution Law:

$$\blacksquare (X')' = X$$

■ Commutative Laws:

$$\blacksquare X + Y = Y + X$$

$$\blacksquare XY = YX$$




■ Distributive laws

$$\blacksquare X(Y + Z) = XY + XZ$$

$$\blacksquare X + YZ = (X + Y) \cdot (X + Z)$$

Associative Laws
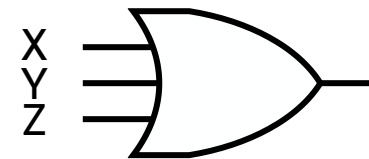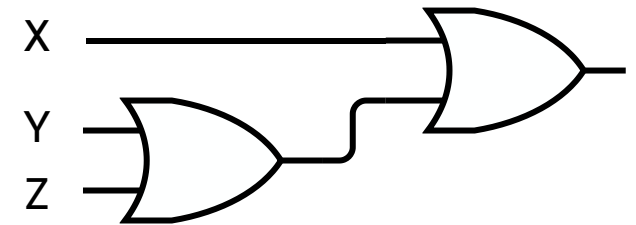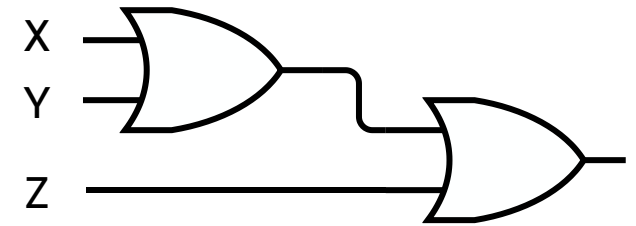
$$(X + Y) + Z = X + (Y + Z) \\ = X + Y + Z$$



Associative Laws

$$(X + Y) + Z = X + (Y + Z) \\ = X + Y + Z$$

$$(XY)Z = X(YZ) \\ = XYZ$$

