



جامعة برج العرب التكنولوجية
BORG AL ARAB TECHNOLOGICAL UNIVERSITY



Digital Engineering

Assoc. Prof. Osama Elnahas, Dr. Dina Abdelhafiz
Dr. Bassant Tolba, Dr. Radwa Rady

Second Year –Information Technology Program
Fall 2025

Lecture 5

DeMorgan's Laws

DeMorgan's Laws:

$$\Rightarrow \overline{(X + Y + Z)} = \bar{X} \cdot \bar{Y} \cdot \bar{Z}$$

$$\Rightarrow \overline{(X \cdot Y \cdot Z)} = \bar{X} + \bar{Y} + \bar{Z}$$

► Replace operators: $+$ $\leftrightarrow$ $\cdot$ and replace each variable with its complement.

$$\Rightarrow \text{Example: } \overline{(X + \bar{Y} + Z)} = \bar{X} \cdot Y \cdot \bar{Z}$$

$$\Rightarrow \text{Example: } \overline{(X \cdot \bar{Y} + Z)} = \overline{(X \cdot \bar{Y})} \cdot \bar{Z} = (\bar{X} + Y) \cdot \bar{Z}$$

Summary

► Did you notice something ??

$X+0 = X$	$X \cdot 1 = X$
$X+1 = 1$	$X \cdot 0 = 0$
$X+X = X$	$X \cdot X = X$
$X+X' = 1$	$X \cdot X' = 0$
$X+Y = Y+X$	$X \cdot Y = Y \cdot X$
$(X+Y)+Z = X+(Y+Z) = X+Y+Z$	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z) = X \cdot Y \cdot Z$
$X \cdot (Y+Z) = X \cdot Y + X \cdot Z$	$X+(Y \cdot Z) = (X+Y) \cdot (X+Z)$
$(X+Y+Z)' = X' \cdot Y' \cdot Z'$	$(X \cdot Y \cdot Z)' = X'+Y'+Z'$

Duality

- Replace operators: $+$ $\leftrightarrow$ $\cdot$ and replace constants $0 \leftrightarrow 1$:
Then you will get new law. (Variables are not changed).

$X+0 = X$	$X \cdot 1 = X$
$X+1 = 1$	$X \cdot 0 = 0$
$X+X = X$	$X \cdot X = X$
$X+X' = 1$	$X \cdot X' = 0$
$X+Y = Y+X$	$X \cdot Y = Y \cdot X$
$(X+Y)+Z = X+(Y+Z) = X+Y+Z$	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z) = X \cdot Y \cdot Z$
$X \cdot (Y+Z) = X \cdot Y + X \cdot Z$	$X+(Y \cdot Z) = (X+Y) \cdot (X+Z)$
$(X+Y+Z)' = X' \cdot Y' \cdot Z'$	$(X \cdot Y \cdot Z)' = X'+Y'+Z'$

Duality

- Replace operators: $+$ $\leftrightarrow$ $\cdot$ and replace constants $0 \leftrightarrow 1$:
Then you will get new law. (Variables are not changed).
- Extra basic laws:

$0+0 = 0$	$1 \cdot 1 = 1$
$1+1 = 1$	$0 \cdot 0 = 0$
$0+1 = 1+0 = 1$	$1 \cdot 0 = 0 \cdot 1 = 0$

Duality

- Given a function: $F = A \cdot \bar{B} + C$
- It is required to find its dual:
 - Replace operators: $+$ $\leftrightarrow$ $\cdot$ and replace constants $0 \leftrightarrow 1$:
Then you will get new law. (Variables are not changed).
 $F^D = ??$

Duality

- Given a function: $F = A \cdot \bar{B} + C$
- It is required to find its dual:
 - Replace operators: $+ \leftrightarrow \cdot$ and replace constants $0 \leftrightarrow 1$:
Then you will get new law. (Variables are not changed).

$$F^D = (A + \bar{B}) \cdot C$$

- It is required to find its complement:
 - DeMorgans Law: Replace operators: $+ \leftrightarrow \cdot$ and replace each variable with its complement.

$$\bar{F} = \overline{(A \cdot \bar{B} + C)} = ??$$

Duality

- Given a function: $F = A \cdot \bar{B} + C$
- It is required to find its dual:
 - Replace operators: $+ \leftrightarrow \cdot$ and replace constants $0 \leftrightarrow 1$:
Then you will get new law. (Variables are not changed).

$$F^D = (A + \bar{B}) \cdot C$$

- It is required to find its complement:
 - DeMorgans Law: Replace operators: $+ \leftrightarrow \cdot$ and replace each variable with its complement.

$$\bar{F} = \overline{(A \cdot \bar{B} + C)} = (\bar{A} + B) \cdot \bar{C}$$

- Did you notice something?? $\bar{F} \leftrightarrow F^D$

Duality

- To change between $\bar{F} \leftrightarrow F^D$: Change each variable to its complement.

- Example: $F = A \cdot \bar{B} + C$

$$F^D = (A + \bar{B}) \cdot \bar{C}$$
$$\bar{F} = \overline{(A \cdot \bar{B} + C)} = (\bar{A} + B) \cdot \bar{C}$$

- Generally:

$$\bar{F}(A, B, C) = F^D(\bar{A}, \bar{B}, \bar{C})$$

Duality

$$\bar{F}(A, B, C) = F^D(\bar{A}, \bar{B}, \bar{C})$$

- Take the complement:

$$F(A, B, C) = \overline{(F^D(\bar{A}, \bar{B}, \bar{C}))}$$

- How to read this ?

- If you have a function $F(A, B, C)$
- Find its dual function $F^D(A, B, C)$
- Complement all the inputs $F^D(\bar{A}, \bar{B}, \bar{C})$
- Complement the output $\overline{(F^D(\bar{A}, \bar{B}, \bar{C}))}$
- You will get the original function $F(A, B, C) = \overline{(F^D(\bar{A}, \bar{B}, \bar{C}))}$

Graphical DeMorgan's Law

Example:


■ If you have a function $F(A, B) = A \cdot B$

■ Find its dual function $F^D(A, B)$
 $= A + B$

■ Complement all the inputs $F^D(\bar{A}, \bar{B})$
 $= \bar{A} + \bar{B}$


■ Complement the output $\overline{(F^D(\bar{A}, \bar{B}))}$
 $= \overline{(\bar{A} + \bar{B})}$

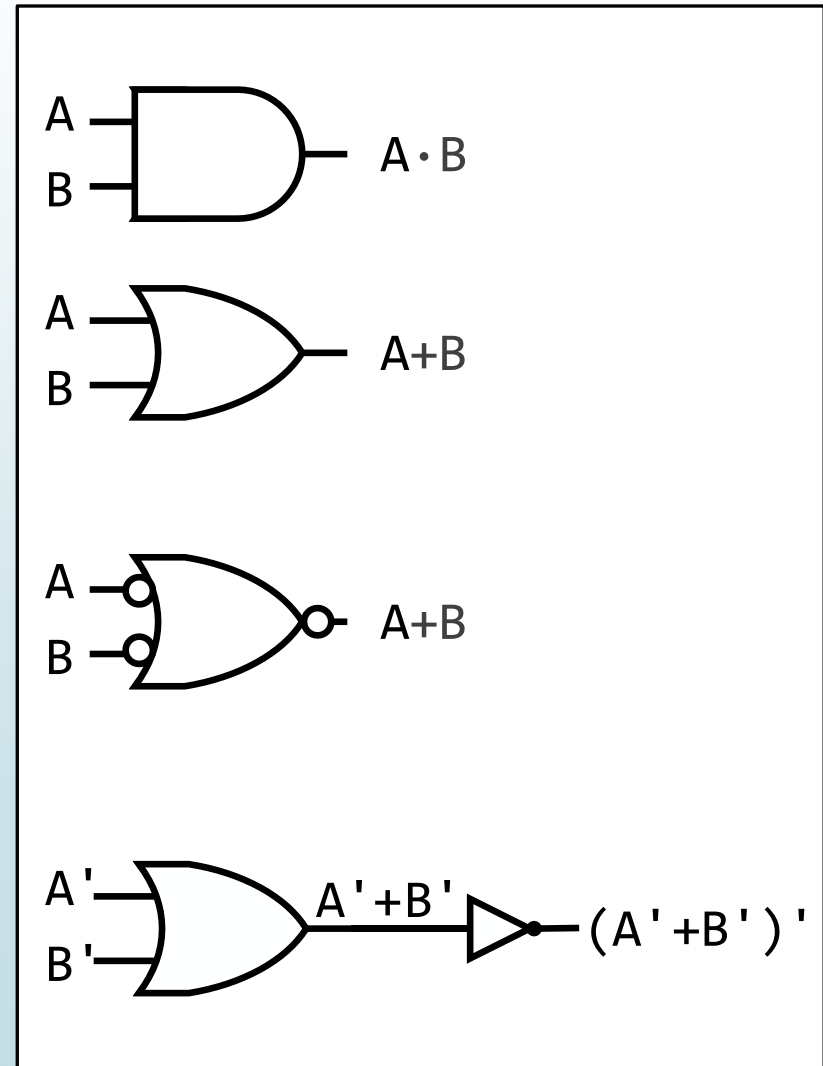■ You will get the original function
 $F(A, B) = \overline{(F^D(\bar{A}, \bar{B}))} = A \cdot B$




Graphical DeMorgan's Law

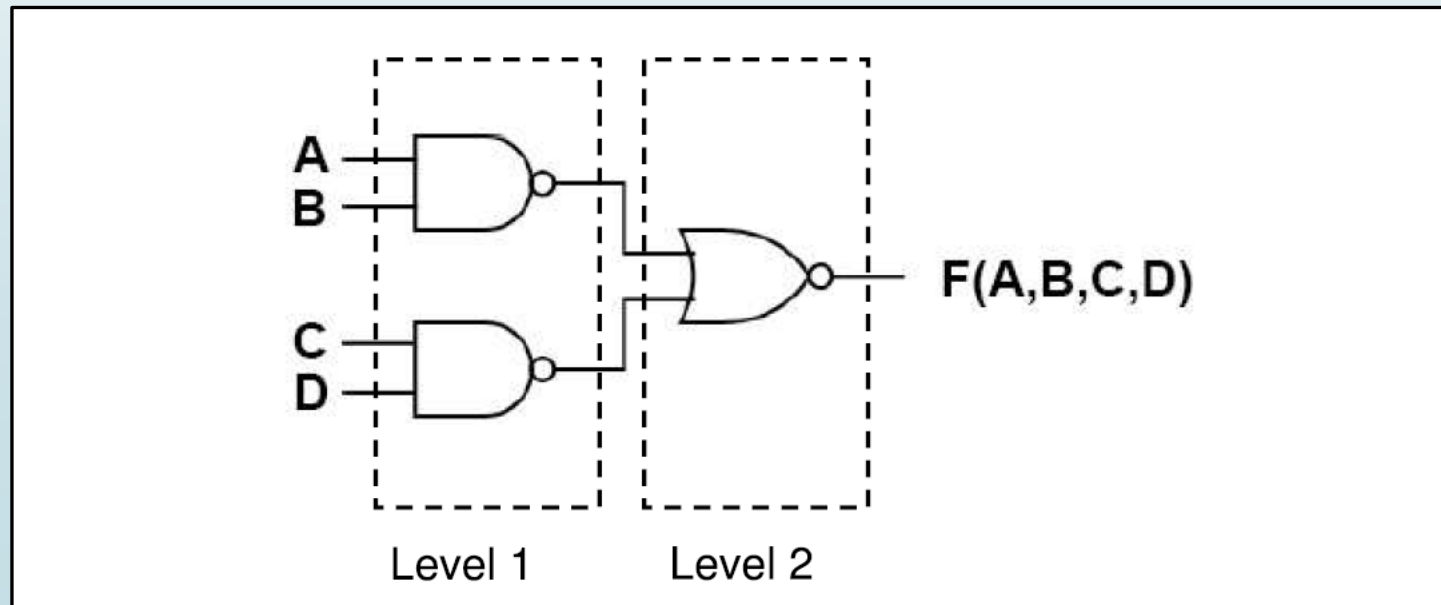- Another example:
 - Given a circuit of multi-level, ignore the equation.
 - Apply Graphical DeMorgans Law on the last level.




Graphical DeMorgan's Law

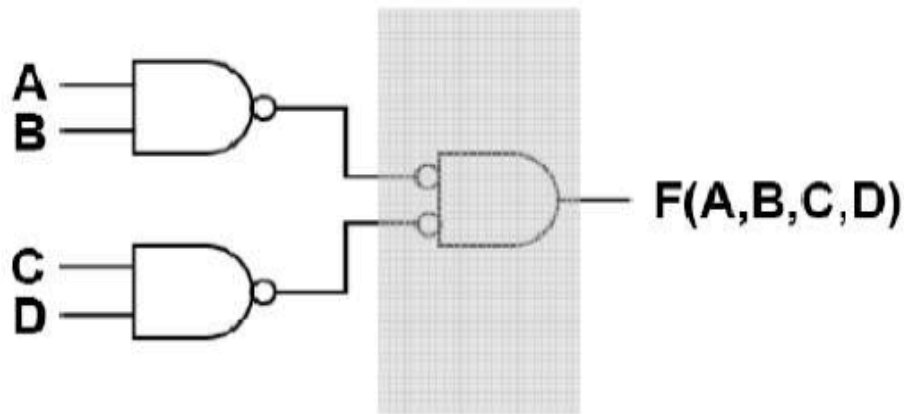- Another example:
 - Flip the OR into AND
 - Add complement circles to inputs.
 - Remove complement circle from output.




Graphical DeMorgan's Law

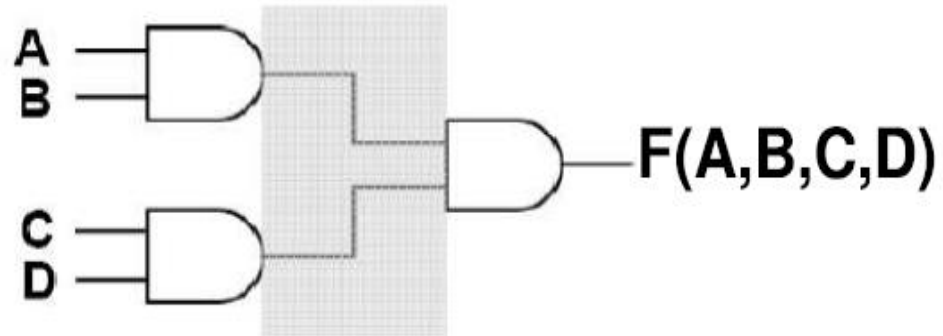- Another example:
 - Flip the OR into AND
 - Add complement circles to inputs.
 - Remove complement circle from output.




Graphical DeMorgan's Law

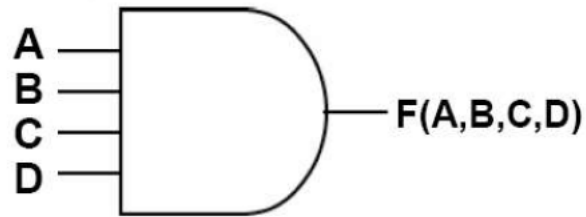- Another example:
 - Flip the OR into AND
 - Add complement circles to inputs.
 - Remove complement circle from output.



Graphical DeMorgan's Law

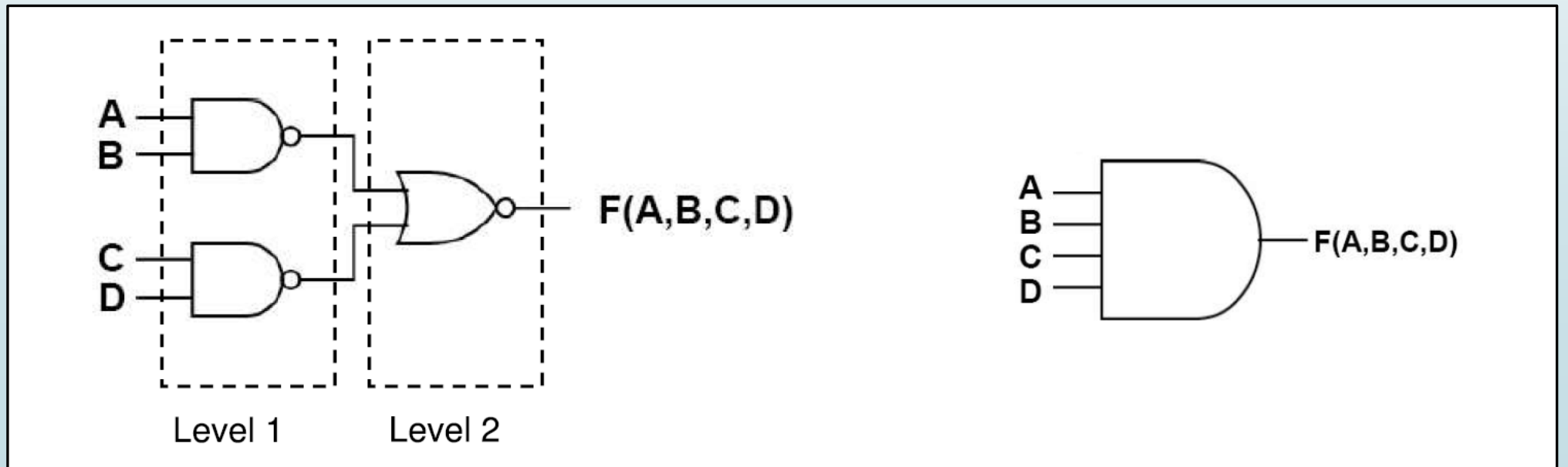- Another example:
 - Then, this multi-level circuit is reduced to single gate.
 - Two different circuits for the same function.
 - This may reduce the cost of implementation.



Simplification Theorems

- Simplification theorem (1):

$$\begin{aligned}X + XY &= X(1+Y) \\&= X \cdot 1 \\&= X\end{aligned}$$

- Apply duality: ??

$$X(X+Y) = X$$

Simplification Theorems

- Simplification theorem (2):

$$\begin{aligned}XY + XY' &= X(Y + Y') \\&= X \cdot 1 \\&= X\end{aligned}$$

- Apply duality:

$$\begin{aligned}(X + Y) \cdot (X + Y') &= X + (Y \cdot Y') \\&= X + 0 \\&= X\end{aligned}$$

Simplification Theorems

- Redundancy theorem:

$$XY + X'Z + YZ = XY + X'Z$$

- The last term is redundant.

- Apply duality: ??

$$(X+Y) \cdot (X' + Z) \cdot (Y+Z) = (X+Y) \cdot (X' + Z)$$

Summary

► Summary part (2):

$X + XY = X$	$X(X+Y) = X$
$XY + XY' = X$	$(X+Y)(X+Y') = X$
$XY + X'Z + YZ = XY + X'Z$	$(X+Y) \cdot (X'+Z) \cdot (Y+Z) = (X+Y) \cdot (X'+Z)$

Circuit Minimization using Boolean Algebra

Circuit Minimization

- How do you think could we simplify these equations ??
- One possible solution is to use Boolean Algebra.
- Consider the sum of products equation:

$$f = A'BC' + A'BC + AB'C + ABC$$

- Search for any two similar terms except one complement ??

$$f = A'BC' + A'BC + AB'C + ABC$$

$$f = A'BC' + A'BC + AB'C + ABC$$

$$f = A'BC' + A'BC + AB'C + ABC$$

Circuit Minimization

- For each group apply the rule $XY + XY' = X(Y + Y') = X$.

$$f = A'BC' + A'BC + AB'C + ABC \rightarrow A'B(C' + C) = A'B$$

$$f = A'BC' + A'BC + AB'C + ABC \rightarrow (A' + A)BC = BC$$

$$f = A'BC' + A'BC + AB'C + ABC \rightarrow A(B' + B)C = AC$$

- If you found two intersecting group, duplicate the common term, applying the rule $X + X = X$:

$$f = A'BC' + A'BC + A'BC + AB'C + ABC + ABC$$

- Group the similar terms:

$$f = (A'BC' + A'BC) + (A'BC + ABC) + (AB'C + ABC)$$

Circuit Minimization

- Group the similar terms:

$$f = (A'BC' + A'BC) + (A'BC + ABC) + (AB'C + ABC)$$

- Apply the rule $XY + XY' = X(Y + Y') = X$, then:

$$f = A'B(C' + C) + (A' + A)BC + A(B' + B)C$$


- Then: $f = A'B + BC + AC$

- Remember the redundancy rule: $XY + X'Z + YZ = XY + X'Z$


- Then: $f = AC + A'B + BC = AC + A'B$

Circuit Minimization

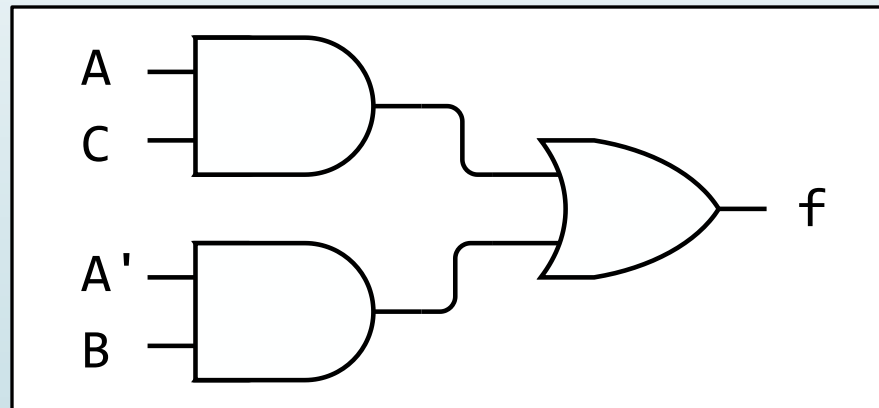- The final simplified function:
- Then: $f = AC + A'B$
- The circuit implementation:




- Compare to the original one.

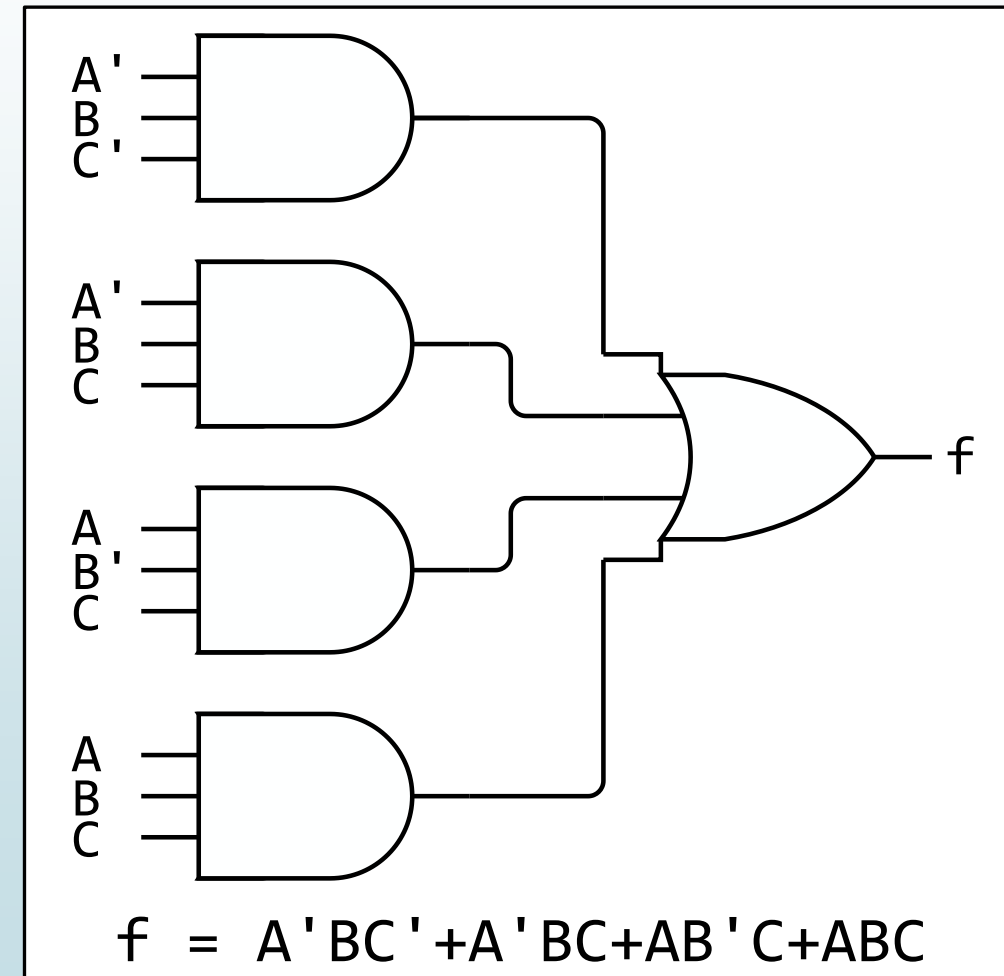


Boolean Algebra

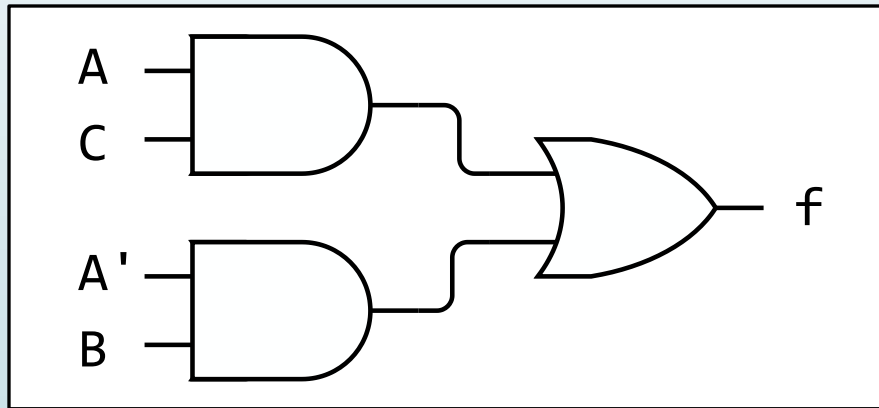- To further reduce the cost: use graphical DeMorgans law on the OR gate:




Boolean Algebra

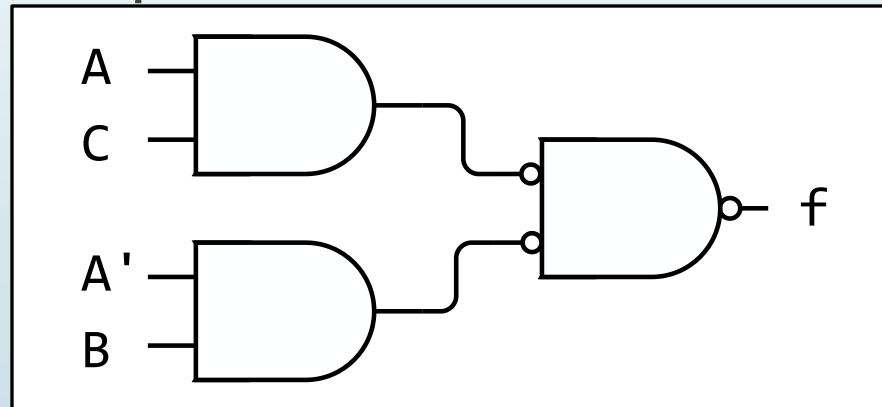- To further reduce the cost: use graphical DeMorgans law on the OR gate:
 - Change the OR to AND and complement all its inputs and output.



Boolean Algebra

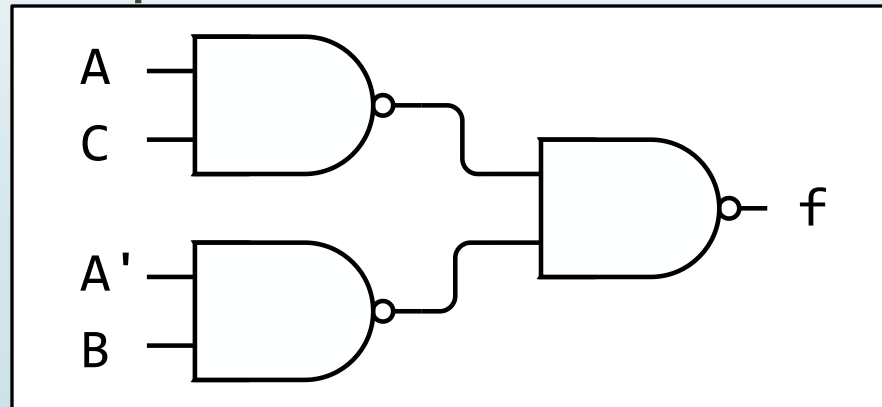- To further reduce the cost: use graphical DeMorgans law on the OR gate:
 - Change the OR to AND and complement all its inputs and output.



- This is a NAND-NAND circuit that is cheaper than the AND-OR circuit, smaller and consumes less power.

Karnaugh Map

Boolean Algebra Minimization

- Recall the prime number detector designed before:

$$f = \sum_{A,B,C} m(2,3,5,7)$$

- Resolve the minterms:

$$f = A'BC' + A'BC + AB'C + ABC$$

$$f = A'B + BC + AC$$

- Search for any two similar terms except one complement.
- Apply the rule $XY + XY' = X(Y + Y') = X$

Karnaugh Map

- The previous example contains only 3 input variables.
- The simplification will be harder and longer with increasing the number of input variables.
- The American scientist Maurice Karnaugh invented his map for doing this grouping visually for faster simplification.

Karnaugh Map

- Assume 3-input variables. Consider the 8 minterms list.
- Assume a table of 8 cells.

A	B	C	Minterms
0	0	0	$A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
0	1	1	$A'BC = m_3$
1	0	0	$AB'C' = m_4$
1	0	1	$AB'C = m_5$
1	1	0	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

- Assume that we will put m_0 in the first cell. Find the similar minterms except one complement ??

$\emptyset$ $A'B'C'$	

A	B	C	Minterms
$\emptyset$	$\emptyset$	$\emptyset$	$A'B'C' = m_0$
$\emptyset$	$\emptyset$	1	$A'B'C = m_1$
$\emptyset$	1	$\emptyset$	$A'BC' = m_2$
$\emptyset$	1	1	$A'BC = m_3$
1	$\emptyset$	$\emptyset$	$AB'C' = m_4$
1	$\emptyset$	1	$AB'C = m_5$
1	1	$\emptyset$	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

- You will find m_1 . Put it beside m_0 . Search for other similar minterm.

0 $A'B'C'$	
1 $A'B'C$	

A	B	C	Minterms
0	0	0	$A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
0	1	1	$A'BC = m_3$
1	0	0	$AB'C' = m_4$
1	0	1	$AB'C = m_5$
1	1	0	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

- You will find m_2 . Put it beside m_0 . Search for other similar minterm.

0 $A'B'C'$	
1 $A'B'C$	
2 $A'BC'$	

A	B	C	Minterms
0	0	0	$A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
0	1	1	$A'BC = m_3$
1	0	0	$AB'C' = m_4$
1	0	1	$AB'C = m_5$
1	1	0	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

- You will find m_4 . Put it beside m_0 . No more minterms similar to m_0 .

0 $A'B'C'$	4 $AB'C'$
1 $A'B'C$	
2 $A'BC'$	

A	B	C	Minterms
0	0	0	$A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
0	1	1	$A'BC = m_3$
1	0	0	$AB'C' = m_4$
1	0	1	$AB'C = m_5$
1	1	0	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

- Similarly, fill in all the table so that each two adjacent cells are different in only one complement.
- Check them ...

$\emptyset$ $A'B'C'$	4 $AB'C'$
1 $A'B'C$	5 $AB'C$
3 $A'BC$	7 ABC
2 $A'BC'$	6 ABC'

A	B	C	Minterms
$\emptyset$	$\emptyset$	$\emptyset$	$A'B'C' = m_{\emptyset}$
$\emptyset$	$\emptyset$	1	$A'B'C = m_1$
$\emptyset$	1	$\emptyset$	$A'BC' = m_2$
$\emptyset$	1	1	$A'BC = m_3$
1	$\emptyset$	$\emptyset$	$AB'C' = m_4$
1	$\emptyset$	1	$AB'C = m_5$
1	1	$\emptyset$	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

► Note the common letter in each row and column. Check it ...

	A'	A	
B'	⁰ A'B'C'	⁴ AB'C'	C'
B'	¹ A'B'C	⁵ AB'C	C
B	³ A'BC	⁷ ABC	C
B	² A'BC'	⁶ ABC'	C'

A	B	C	Minterms
0	0	0	A'B'C' = m ₀
0	0	1	A'B'C = m ₁
0	1	0	A'BC' = m ₂
0	1	1	A'BC = m ₃
1	0	0	AB'C' = m ₄
1	0	1	AB'C = m ₅
1	1	0	ABC' = m ₆
1	1	1	ABC = m ₇

Karnaugh Map

► Note the common letter in each row and column. Check it ...

	A'	A	
B'	⁰ A'B'C'	⁴ AB'C'	C'
	¹ A'B'C	⁵ AB'C	
B	³ A'BC	⁷ ABC	C
	² A'BC'	⁶ ABC'	

A	B	C	Minterms
0	0	0	$A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
0	1	1	$A'BC = m_3$
1	0	0	$AB'C' = m_4$
1	0	1	$AB'C = m_5$
1	1	0	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

- The adjacent cells are different in only one complement. So, we can group any two adjacent cells.

B'	A'	A	C'
	$\emptyset$ $A'B'C'$	4 $AB'C'$	
B	1 $A'BC$	5 $AB'C$	C
	3 $A'BC$	7 ABC	
B	2 $A'BC'$	6 ABC'	C'
	3 $A'BC$	7 ABC	

A	B	C	Minterms
$\emptyset$	$\emptyset$	$\emptyset$	$A'B'C' = m_{\emptyset}$
$\emptyset$	$\emptyset$	1	$A'B'C = m_1$
$\emptyset$	1	$\emptyset$	$A'BC' = m_2$
$\emptyset$	1	1	$A'BC = m_3$
1	$\emptyset$	$\emptyset$	$AB'C' = m_4$
1	$\emptyset$	1	$AB'C = m_5$
1	1	$\emptyset$	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

► Example: $A'B'C + AB'C = B'C$

► The result is the common letters in the group.

B'	A'	A	C'
	0 A'B'C'	4 AB'C'	
B	1 A'B'C	5 AB'C	C
	3 A'BC	7 ABC	
	2 A'BC'	6 ABC'	C'

A	B	C	Minterms
0	0	0	$A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
0	1	1	$A'BC = m_3$
1	0	0	$AB'C' = m_4$
1	0	1	$AB'C = m_5$
1	1	0	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

► We can also group 4 cells. Example:

$$(A'B'C' + AB'C') + (A'B'C + AB'C) = B'C + B'C' = B'$$

		A'	A	
B'		0	4	
		A'B'C'	AB'C'	C'
B		1	5	C
		A'B'C	AB'C	
		3	7	
		A'BC	ABC	
		2	6	
		A'BC'	ABC'	

A	B	C	Minterms
0	0	0	$A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
0	1	1	$A'BC = m_3$
1	0	0	$AB'C' = m_4$
1	0	1	$AB'C = m_5$
1	1	0	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

- This table is the Karnaugh Map (K-map).
- We distributed the input side of truth table.

	A'	A	
B'	0 A'B'C'	4 AB'C'	C'
	1 A'B'C	5 AB'C	C
B	3 A'BC	7 ABC	
	2 A'BC'	6 ABC'	C'

A	B	C	Minterms
0	0	0	$A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
0	1	1	$A'BC = m_3$
1	0	0	$AB'C' = m_4$
1	0	1	$AB'C = m_5$
1	1	0	$ABC' = m_6$
1	1	1	$ABC = m_7$

Karnaugh Map

- Replace each input with its corresponding output.
- Note the order of ones and zeros.

	A'	A	
B'	0 0	4 0	C'
	1 0	5 1	
B	3 1	7 1	C
	2 1	6 0	

A	B	C	Minterms	f
0	0	0	$A'B'C' = m_0$	0
0	0	1	$A'B'C = m_1$	0
0	1	0	$A'BC' = m_2$	1
0	1	1	$A'BC = m_3$	1
1	0	0	$AB'C' = m_4$	0
1	0	1	$AB'C = m_5$	1
1	1	0	$ABC' = m_6$	0
1	1	1	$ABC = m_7$	1

Karnaugh Map

- Previously, we considered only the active minterms.
- Now, we will consider only the ones inside the map.

		A'	A	c'
B'	0	0	0	
	1	0	1	c
B	3	1	1	
	2	1	0	c'

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Karnaugh Map

► Give the letters of this group:

► $f = ??$

	A'	A	
B'	0 0	4 0	C'
	1 0	5 1	C
B	3 1	7 1	
	2 1	6 0	C'

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Karnaugh Map

► Give the letters of this group:

► $f = AC + ??$

	A'	A	
B'	0 0	4 0	C'
	1 0	5 1	C
B	3 1	7 1	
	2 1	6 0	C'

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Karnaugh Map

► This is the only left group, do not consider it. We have all 1s.

► $f = AC + A'B$

	A'	A	
B'	0 0	4 0	C'
	1 0	5 1	C
B	3 1	7 1	
	2 1	6 0	C'

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Karnaugh Map

► This is the final simplified equation. Compare with before.

► $f = AC + A'B$

		A'	A	c'
B'	0	0	0	
	1	0	1	c
B	3	1	1	
	2	1	0	c'

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Steps Summary

- Given a truth table, it is required to find its equation.
- Draw the Karnaugh Map for 3-inputs

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

	A'	A	
B'	0	4	C'
	1	5	
B	3	7	C
	2	6	C'

Steps Summary

- Given a truth table, it is required to find its equation.
- Draw the Karnaugh Map for 3-inputs
- Put the function output inside the cells.
- Find the minimum number of the largest groups that cover all the ones.
- Groups must be 2^n elements, i.e.: 1,2,4,8
- The equations is the summation of these groups letters.
- $f = AC + A'B$

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

	A'	A	
	0	4	C'
B'	0	0	
	1	5	
	0	1	C
	3	7	
	1	1	
B	2	6	C'
	0	0	

Grouping Notes

- Consider this case. You have 2 options for grouping.
- Select the minimum number of the largest groups.
- This leads to the result without extra simplification.

$$f = AB' + AB = A$$

	A'	A	
B'	⁰ 0	⁴ 1	C'
	¹ 0	⁵ 1	C
B	³ 0	⁷ 1	C
	² 0	⁶ 1	C'



$$f = A$$

	A'	A	
B'	⁰ 0	⁴ 1	C'
	¹ 0	⁵ 1	C
B	³ 0	⁷ 1	C
	² 0	⁶ 1	C'



Grouping Notes

- Consider this case. You have 2 options for grouping.
- Select the minimum number of the largest groups.
- This leads to the result without extra simplification.
- $f = ? + ?$



	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	
B	3 1	7 1	C
	2 0	6 1	C'



	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	
B	3 1	7 1	C
	2 0	6 1	C'

Grouping Notes

- Consider this case. You have 2 options for grouping.
- Select the minimum number of the largest groups.
- This leads to the result without extra simplification.
- $f = A + A' C$

	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	C
B	3 1	7 1	C
	2 0	6 1	C'



$f = ? + ?$

	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	C
B	3 1	7 1	C
	2 0	6 1	C'



Grouping Notes

- Consider this case. You have 2 options for grouping.
- Select the minimum number of the largest groups.
- This leads to the result without extra simplification.
- $f = A + A' C$

	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	C
B	3 1	7 1	C
	2 0	6 1	C'



	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	C
B	3 1	7 1	C
	2 0	6 1	C'



Grouping Notes

- Consider this case. You have 2 options for grouping.
- Select the minimum number of the largest groups.
- This leads to the result without extra simplification.
- $f = A + A' C = (A + A') (A + C) = A + C$

	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	C
B	3 1	7 1	C
	2 0	6 1	C'



	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	C
B	3 1	7 1	C
	2 0	6 1	C'



Grouping Notes

- Consider this case. You have 2 options for grouping.
- Select the minimum number of the largest groups.
- This leads to the result without extra simplification.
- $f = A + A' C = (A + A') (A + C) = A + C$

	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	
B	3 1	7 1	C
	2 0	6 1	C'

	A'	A	
B'	0 0	4 1	C'
	1 1	5 1	
B	3 1	7 1	C
	2 0	6 1	C'

Two Inputs


- In case of 2- input functions. It might be easier to resolve it without Karnaugh map.
- Consider the given truth table.
- Using minterms only: $f = A'B' + A'B = A'$
- However, you could use the Karnaugh map in this way:
 - Draw the 2-inputs K-map like this:
 - $f = A'$

A	B	f
0	0	1
0	1	1
1	0	0
1	1	0

	A'	A
B'	0 1	2 0
B	1 1	3 0

Examples from Textbook

$$\blacksquare f = ab + c'$$

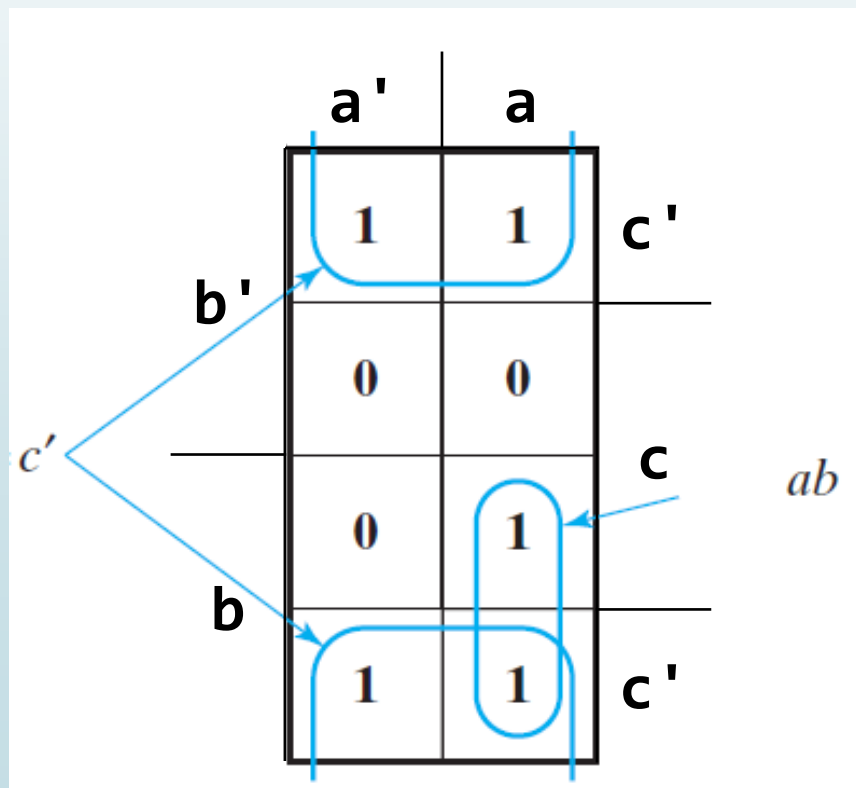

Examples from Textbook

■ The clear cells are zeros by default.

■ $f = xy + x'z + yz = xy + x'z$

$f = x'z + xy$

